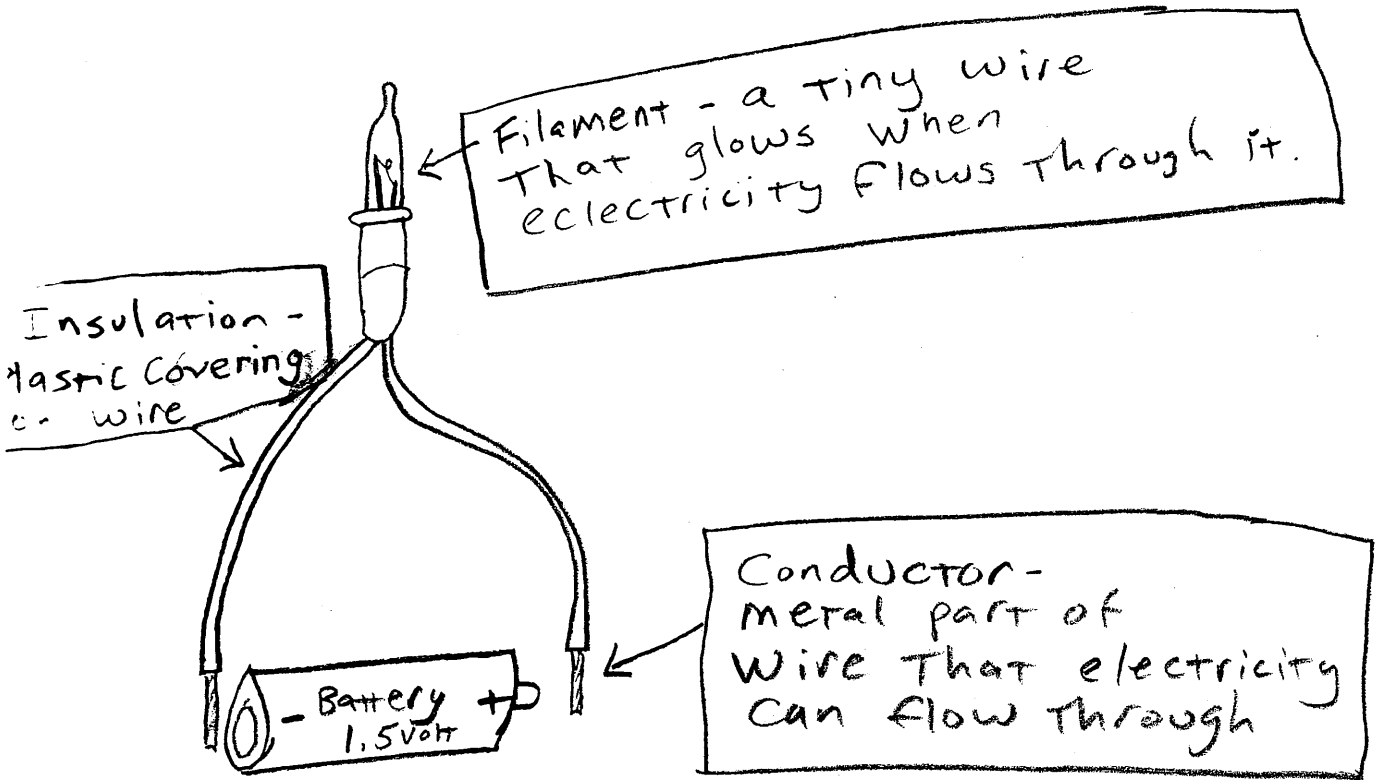


# Electric lights



## Light a tree light!

Touch both conductors on a tree light to the two ends of a battery.

**Circuit:**  
Electricity must flow in a circle - out of one end of battery, through the light, and back to the other end of the battery.

